

CLASS: BTech  
BRANCH: EEE

SEMESTER : III  
SESSION : MO/2022

SUBJECT: EE201 ELECTRICAL MEASUREMENT AND INSTRUMENTATION  
TIME: 03 Hours  
FULL MARKS: 50

INSTRUCTIONS:

1. The question paper contains 5 questions each of 10 marks and total 50 marks.
2. Attempt all questions.
3. The missing data, if any, may be assumed suitably.
4. Tables/Data handbook/Graph paper etc., if applicable, will be supplied to the candidates

- Q.1(a) Define the term scale span and give example. [2]  
Define the term sensitivity drift and draw the graph. CO 1, BL 2
- Q.1(b) Three resistors have the following ratings:  $R_1 = 200 \Omega \pm 5\%$ ,  $R_2 = 100 \Omega \pm 5\%$  and  $R_3 = 50 \Omega \pm 5\%$ . [3]  
Determine the limiting error in percentage and in ohm if the above resistances are connected in parallel. CO 1, BL 5
- Q.1(c) Define primary and secondary standards. [5]  
A batch of colour coded resistors of value  $5.6 \text{ k}\Omega$  were measured and were found to have the following values: 5.75, 5.60, 5.65, 5.50, 5.70, 5.55, 5.80, 5.55  $\text{k}\Omega$ . Determine the mean and standard deviation. CO 1, BL 5
- Q.2(a) The coil of a measuring instrument has a resistance of  $1 \Omega$  and the instrument has a full scale deflection of 250 V when a resistance of  $4999 \Omega$  is connected in series with it. Find (a) the current range of the instrument when used as an ammeter with the coil connected across a shunt of  $1/499 \Omega$  and (b) the value of the shunt resistance for the instrument to give a full scale deflection of 50 A. [2]  
CO 2, BL 3
- Q.2(b) Describe the construction and working of PMMC instrument. Derive the equation for deflection if the instrument is spring controlled. [3]  
CO 2, BL 3
- Q.2(c) Describe the constructional details and working of a single phase electrodynamicometer type of power factor meter for measurement of power factor. [5]  
CO 2, BL 4
- Q.3(a) Draw the circuit diagram of a basic slide wire potentiometer and state in short the procedure for standardization of the potentiometer. [2]  
CO 3, BL 3
- Q.3(b) Describe the Murray Loop test for localization of short circuit faults in cables. [3]  
CO 3, BL 3
- Q.3(c) Describe the working of a low voltage Schering bridge. Derive the equation for capacitance. Draw the phasor diagram of the bridge under conditions of balance. [5]  
CO 3, BL 4
- Q.4(a) Compare between analog and digital instruments. (2 points) [2]  
CO 4, BL 2
- Q.4(b) What is the function of a time base generator in a CRO. Explain with a circuit how a time base is generated in a CRO. [3]  
CO 4, BL 3
- Q.4(c) What is an XY recorder. Explain with a suitable diagram, the working of an XY recorder. Write any two of its applications. [5]  
CO 4, BL 3
- Q.5(a) Distinguish between a primary and a secondary transducer with an example. [2]  
CO 5, BL 2
- Q.5(b) Explain how a capacitive transducer can be used for measurement of linear and rotational displacement (one method each). [3]  
CO 5, BL 3
- Q.5(c) Describe the construction, theory and working of thermocouples. [5]  
CO 5, BL 3

::::22/11/2022::::E